


DANCING WITH YOUR THUMBS – ANKITH TUNUGUNTLA

EE – 271 LAB #8

The game:

Dancing with your thumbs involves using your thumbs to hit different keys on the DE1SoC to perfectly time the tiles moving upward. You earn points with each key pressed in sync with the moving tiles under a time limit of 30 seconds.

Controls:

 

Gameplay:

Turn on SW9 to start the game where the tiles shall move at a default speed. You can turn on SW8 to view the high score at any time. SW7 clears the high score and resets it to zero. When the game starts, a thirty second timer counts down beyond which the game will not count the score any further.

You can use:

- SW[6:0] – to turn on different levels of speed. The game will run at a particular speed when a particular switch is on. If no switch in this range is switched on, then the game runs at the default speed.
- KEY[3:0] – to press when a tile moves to the top of the respective bank. Each key corresponds to a 16x4 section on the LED array. Key 3 corresponds to the first section, Key 2 corresponds to the second section, and so on and so forth.

Scoring:

For every tile you match correctly with the appropriate key, you gain +2 points. Matching incorrectly by a row with a key press shall gain you +1 points. Matching incorrectly by not pressing a key when the tile is at the top or pressing incorrectly will earn you a deduction of 2 points.

Extra features absent from the spec:

- Timer – 30 second timer that counts to 0.
- High score and the option to clear it

Market and Usability Analysis:

- Usability and ergonomics – I have used the entire LED array split into four different parts which involves tiles in alternating colors of red and green so the user can see the difference between the banks of tiles. The keys when pressed turn the top row orange to indicate the key being pressed. The option to change speeds, see the scores on the hexes add to the ergonomics of the entire design.
- Suitability for goals – I have made a game for a project, so the system is indeed fun and the game play is logical. The addition of a high score and a time limit induces a competitive nature within the game.
- Cost and resource utilization – The resource utilization is high due to several modules, LFSRs, LED modules, etc.


Node	Combinational ALUTs	Dedicated Logic Resources
748 (26)		147 (0)
28 (28)		4 (4)

- Public Health, safety and welfare – the system poses no risk or injury and is a low-voltage game. The game is a positive harmless recreational activity and appeals to all ethnics, cultures and age groups and does not require any prior knowledge other than the instructions given in this manual.

Time taken:

3 days approx. for development of idea/schematic, coding, simulations and debugging

Block diagram:

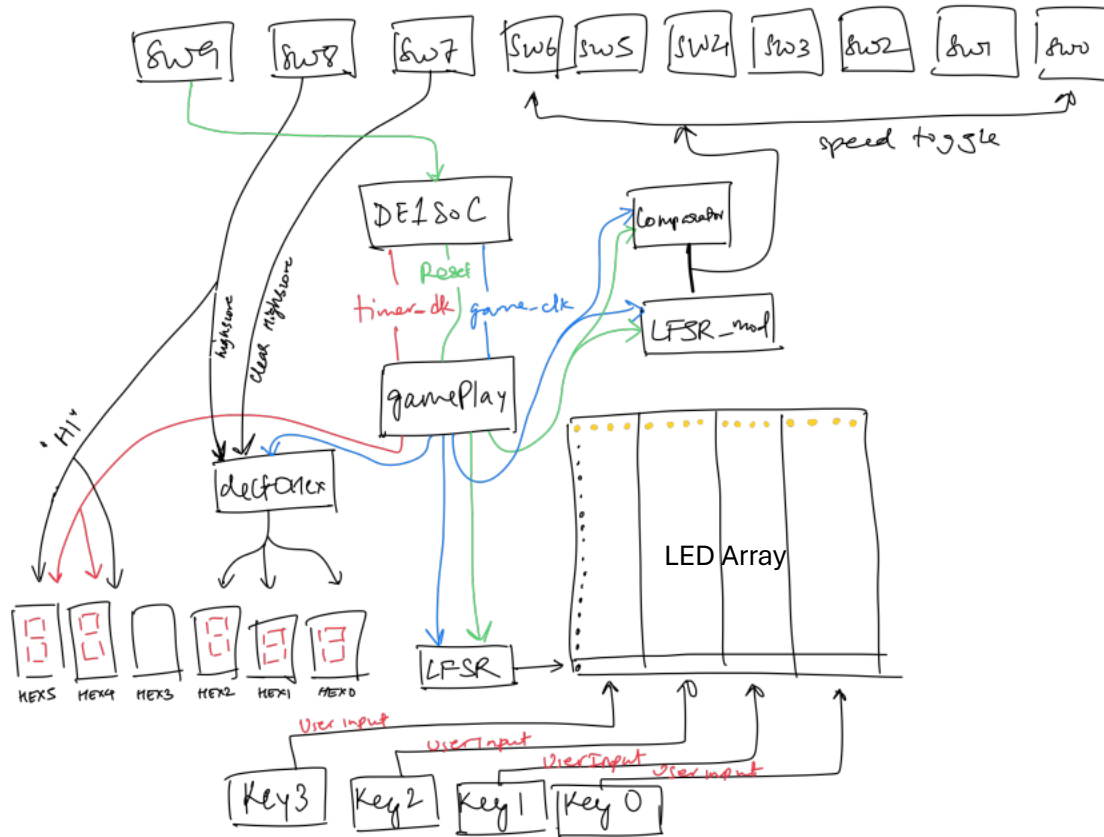

```

module gamePlay(
    input logic clk,      // Clock[22]
    input logic timer_clk, // Clock[25]
    input logic reset,
    input logic highScoreDisplay,
    input logic clearHighScore,
    input logic [6:0] speedSW,
    input logic key3,
    input logic key2,
    input logic key1,
    input logic key0,
    output logic [15:0][15:0] RedPixels,
    output logic [15:0][15:0] GrnPixels,
    output logic [6:0] hex2,
    output logic [6:0] hex1,
    output logic [6:0] hex0,
    output logic [6:0] hex5,
    output logic [6:0] hex4,
    output logic [6:0] hex3
);

    assign hex3 = 7'b1111111; // HEX 3 NOT USED

    // LFSR FOR TILE PATTERN
    logic [15:0] lfsr_pattern;
    LFSR lfsr_inst (.Out(lfsr_pattern), .clk(clk), .rst(reset));

    logic [8:0] score; // game score
    logic [8:0] highScore; // all-time highscore initialized to 0

```

```

logic [6:0] hex2_2, hex1_2, hex0_2; // hexes for score

logic [6:0] hex2_1, hex1_1, hex0_1; // hexes for high score


logic [15:0][15:0] nextRedPixels, nextGrnPixels; // updated red and green pixels


// Timer variables

logic [4:0] timer;

logic [6:0] hex5_disp, hex4_disp; // hexes for timer


    decToHex timer_to_hex (.score({4'b0, timer}), .hex2(), .hex1(hex5_disp), .hex0(hex4_disp)); //
conversion of timer to hex display


// Score to hex conversion

    decToHex dh1 (.score(score), .hex2(hex2_1), .hex1(hex1_1), .hex0(hex0_1)); // conversion of
score to hex display

    decToHex dh2 (.score(highScore), .hex2(hex2_2), .hex1(hex1_2), .hex0(hex0_2)); // conversion
of high score to hex display


logic gameOver;


logic [9:0] lfsr_output; // LFSR FOR SPEED TOGGLE

logic speed; // speed signal


LFSR_mod l (.Clock(clk), .Reset(reset), .Out(lfsr_output));

comparator comp1 (.a({3'b0, speedSW[6:0]}), .b(lfsr_output), .out(speed));


logic [10:0] counter;


// Timer decrement logic

```

```

always_ff @(posedge timer_clk or posedge reset) begin
    if (reset) begin
        timer <= 30;
    end else begin

        if (timer != 0) begin
            timer <= timer - 1;
        end
    end
end

// Main logic with clk for key responsiveness and tile generation
always_ff @(posedge clk or posedge reset) begin
    if (reset) begin
        nextRedPixels <= '{default: 16'b0};
        nextGrnPixels <= '{default: 16'b0};
        RedPixels <= '{default: 16'b0};
        GrnPixels <= '{default: 16'b0};
        score <= 0;
    end else begin
        // Shift pixels up
        for (int i = 1; i < 16; i++) begin
            nextRedPixels[i-1] = RedPixels[i];
            nextGrnPixels[i-1] = GrnPixels[i];
        end

        // Update RedPixels and GrnPixels
        RedPixels <= nextRedPixels;
        GrnPixels <= nextGrnPixels;
    end
end

```

```

// Key handling

if (~key3) begin
    GrnPixels[0][15:12] <= 4'b1111;
    RedPixels[0][15:12] <= 4'b1111;
end

if (~key2) begin
    GrnPixels[0][11:8] <= 4'b1111;
    RedPixels[0][11:8] <= 4'b1111;
end

if (~key1) begin
    GrnPixels[0][7:4] <= 4'b1111;
    RedPixels[0][7:4] <= 4'b1111;
end

if (~key0) begin
    GrnPixels[0][3:0] <= 4'b1111;
    RedPixels[0][3:0] <= 4'b1111;
end

// Assign new random pattern to the first row
nextRedPixels[15][15:12] <= {4{lfsr_pattern[0]}};
nextGrnPixels[15][11:8] <= {4{lfsr_pattern[4]}};
nextRedPixels[15][7:4] <= {4{lfsr_pattern[8]}};
nextGrnPixels[15][3:0] <= {4{lfsr_pattern[12]}};

// Light hit detection
if ((RedPixels[0][15:12] == 4'b1111 & ~key3) ||

```

```

    (GrnPixels[0][11:8] == 4'b1111 & ~key2) ||
    (RedPixels[0][7:4] == 4'b1111 & ~key1) ||
    (GrnPixels[0][3:0] == 4'b1111 & ~key0)) begin
    score <= score + 2;

                                //highScore <= highScore + 2;
end else if ((RedPixels[1][15:12] == 4'b1111 & RedPixels[0][15:12] == 4'b0000 & ~key3) ||
    (GrnPixels[1][11:8] == 4'b1111 & GrnPixels[0][11:8] == 4'b0000 & ~key2) ||
    (RedPixels[1][7:4] == 4'b1111 & RedPixels[0][7:4] == 4'b0000 & ~key1) ||
    (GrnPixels[1][3:0] == 4'b1111 & GrnPixels[0][3:0] == 4'b0000 & ~key0)) begin
    score <= score + 1;

                                //highScore <= highScore + 1;
end else if (((RedPixels[1][15:12] == 4'b0000 & RedPixels[0][15:12] == 4'b0000 & ~key3) ||
    (GrnPixels[1][11:8] == 4'b0000 & RedPixels[0][11:8] == 4'b0000 & ~key2) ||
    (RedPixels[1][7:4] == 4'b0000 & RedPixels[0][7:4] == 4'b0000 & ~key1) ||
    (GrnPixels[1][3:0] == 4'b0000 & RedPixels[0][3:0] == 4'b0000 & ~key0)) & score >= 2)
begin
    score <= score - 2;

                                //highScore <= highScore - 2;

end

if (clearHighScore & ~highScoreDisplay & ~reset) begin
    highScore <= 0;
end else if (score > highScore) begin
    highScore <= score;
end
end
end

always_comb begin

```



```
    if (highScoreDisplay) begin
        // Display high score

        hex5 = 7'b0001001; // 'H'
        hex4 = 7'b1001111; // 'I'

        hex2 = hex2_2;
        hex1 = hex1_2;
        hex0 = hex0_2;
    end else begin
        // Normal game play display

        hex5 = hex5_disp;
        hex4 = hex4_disp;
        hex2 = hex2_1;
        hex1 = hex1_1;
        hex0 = hex0_1;
    end
end

endmodule
```

```
module gamePlay_testbench();
```

```
    // Inputs
    reg clk;
    reg timer_clk;
    reg reset;
    reg highScoreDisplay;
    reg clearHighScore;
    reg [6:0] speedSW;
    reg key3;
```

```
reg key2;
```

```
reg key1;
```

```
reg key0;
```

```
// Outputs
```

```
wire [15:0][15:0] RedPixels;
```

```
wire [15:0][15:0] GrnPixels;
```

```
wire [6:0] hex2;
```

```
wire [6:0] hex1;
```

```
wire [6:0] hex0;
```

```
wire [6:0] hex5;
```

```
wire [6:0] hex4;
```

```
wire [6:0] hex3;
```

```
gamePlay dut (
```

```
    .clk(clk),
```

```
    .timer_clk(timer_clk),
```

```
    .reset(reset),
```

```
    .highScoreDisplay(highScoreDisplay),
```

```
    .clearHighScore(clearHighScore),
```

```
    .speedSW(speedSW),
```

```
    .key3(key3),
```

```
    .key2(key2),
```

```
    .key1(key1),
```

```
    .key0(key0),
```

```
    .RedPixels(RedPixels),
```

```
    .GrnPixels(GrnPixels),
```

```
    .hex2(hex2),
```

```
.hex1(hex1),  
.hex0(hex0),  
.hex5(hex5),  
.hex4(hex4),  
.hex3(hex3)  
);
```

```
// Clock generation
```

```
initial begin
```

```
    clk = 0;
```

```
    forever #5 clk = ~clk; // 100 MHz clock
```

```
end
```

```
initial begin
```

```
    timer_clk = 0;
```

```
    forever #50 timer_clk = ~timer_clk; // Slower clock for timer
```

```
end
```

```
// Initial setup and stimulus
```

```
initial begin
```

```
    // Initialize Inputs
```

```
    reset = 1;
```

```
    highScoreDisplay = 0;
```

```
    clearHighScore = 0;
```

```
    speedSW = 7'b0;
```

```
    key3 = 1;
```

```
    key2 = 1;
```

```
    key1 = 1;
```

```
    key0 = 1;
```

// Wait for global reset to finish

#100;

reset = 0;

// Simulate key presses

#100;

key3 = 0; #20; key3 = 1; // Press and release key3

#100;

key2 = 0; #20; key2 = 1; // Press and release key2

#100;

key1 = 0; #20; key1 = 1; // Press and release key1

#100;

key0 = 0; #20; key0 = 1; // Press and release key0

// Simulate high score display

#200;

highScoreDisplay = 1;

#100;

highScoreDisplay = 0;

// Simulate clear high score

#200;

clearHighScore = 1;

#100;

clearHighScore = 0;

// Simulate speed switch changes

```

#200;

speedSW = 7'b0111111;

#100;

speedSW = 7'b1011111;

#100;

speedSW = 7'b1101111;

#100;

speedSW = 7'b1110111;

#100;

speedSW = 7'b1111011;

#100;

speedSW = 7'b1111101;

#100;

speedSW = 7'b1111110;


// Finish simulation

#500;

$finish;

end


// Monitor outputs

initial begin

    $monitor("Time: %0t, score: %d, highScore: %d, timer: %d, hex0: %b, hex1: %b, hex2: %b,
hex4: %b, hex5: %b",

        $time, dut.score, dut.highScore, dut.timer, hex0, hex1, hex2, hex4, hex5);

end


endmodule

```

```

module DE1_SoC (
    output logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5,
    output logic [9:0] LEDR,
    input logic [3:0] KEY,
    input logic [9:0] SW,
    output logic [35:0] GPIO_1,
    input logic CLOCK_50
);

    // Turn off HEX displays


    // Clock divider
    logic [31:0] Clock;
    logic SYSTEM_CLOCK;
    logic game_clk;
        logic timer_clk;
    clock_divider divider (.clock(CLOCK_50), .divided_clocks(Clock));
    assign SYSTEM_CLOCK = Clock[14]; // 1526 Hz clock signal
        assign timer_clk = Clock[25];


    // Speed control logic
    logic [4:0] speed;

    always_comb begin
        if (SW[6]) begin

```

```
    speed = 5'd19;
end else if (SW[5]) begin
    speed = 5'd20;
end else if (SW[4]) begin
    speed = 5'd21;
end else if (SW[3]) begin
    speed = 5'd22;
end else if (SW[2]) begin
    speed = 5'd23;
end else if (SW[1]) begin
    speed = 5'd24;
end else if (SW[0]) begin
    speed = 5'd25;
end else begin
    speed = 5'd22; // Default speed if no switch is turned on
end
end
```

```
    assign game_clk = Clock[speed];
```

```
// LED board driver
```

```
logic [15:0][15:0] RedPixels; // 16 x 16 array representing red LEDs
```

```
logic [15:0][15:0] GrnPixels; // 16 x 16 array representing green LEDs
```

```
logic reset; // reset signal
```

```
assign reset = ~SW[9];
```

```
// LED Driver instantiation
```

```
LEDDriver Driver (  
    .GPIO_1(GPIO_1),  
    .CLK(SYSTEM_CLOCK),  
    .RST(reset),  
    .EnableCount(1'b1),  
    .RedPixels(RedPixels),  
    .GrnPixels(GrnPixels)  
);
```

```
    //gamePlay g (.clk(game_clk), .reset, .highScoreDisplay(SW[8]),  
    .clearHighScore(SW[7]), .key3(KEY[3]), .key2(KEY[2]), .key1(KEY[1]), .key0(KEY[0]), .RedPixels,  
    .GrnPixels, .hex2(HEX2), .hex1(HEX1), .hex0(HEX0), .hex5(HEX5), .hex4(HEX4), .hex3(HEX3));
```

```
    gamePlay g (.clk(game_clk), .timer_clk, .reset, .highScoreDisplay(SW[8]),  
    .clearHighScore(SW[7]), .speedSW(SW[6:0]), .key3(KEY[3]), .key2(KEY[2]), .key1(KEY[1]),  
    .key0(KEY[0]), .RedPixels, .GrnPixels, .hex2(HEX2), .hex1(HEX1), .hex0(HEX0), .hex5(HEX5),  
    .hex4(HEX4), .hex3(HEX3));
```

```
endmodule
```



```
module LFSR_mod(Clock, Reset, Out);
```

```
input logic Clock, Reset;
```

```
output logic [9:0] Out;
```

```
logic xnor_out;
```

```
assign xnor_out = (Out[3] ~^ Out[0]);
```

```
logic LFSR;
```

```
always_ff @(posedge Clock) begin
```

```
    if (Reset)
```

```
        Out <= 10'b0;
```

```
    else
```

```
        Out <= {xnor_out, Out[9:1]};
```

```
    end
```

```
endmodule
```

```
module LFSR_mod_testbench();
```

```
    logic clk, Reset;
```

```
    logic [9:0] Out;
```

```
    LFSR_mod l(.Clock(clk), .Reset, .Out);
```

```
    parameter CLOCK_PERIOD=100;
```

```
    initial begin
```

```
        clk <= 0;
```

```
        forever #(CLOCK_PERIOD/2) clk <= ~clk; // Forever toggle the clock
```

```
    end
```

```
// Set up the inputs to the design. Each line is a clock cycle.  
  
initial begin  
  
    repeat(1); @(posedge clk);  
  
    Reset <= 1; repeat(1) @(posedge clk); // Always reset FSMs at start  
  
    Reset <= 0; repeat(100) @(posedge clk);  
  
    $stop; // End the simulation.  
  
end  
  
endmodule
```

```

module LFSR(Out, clk, rst);

    input logic clk, rst;
    output logic [15:0] Out;

    logic xnor_out;
    assign xnor_out = (Out[0] ^ Out[1] ^ Out[3] ^ Out[12]);

    always_ff @(posedge clk) begin
        if (rst)
            Out <= 16'b0;
        else
            Out <= {xnor_out, Out[15:1]};
        end
    endmodule

```

```

module LFSR_testbench();

    logic clk, Reset;
    logic [15:0] Out;
    LFSR l(.clk, .rst(Reset), .Out);

    parameter CLOCK_PERIOD=100;

    initial begin
        clk <= 0;
        forever #(CLOCK_PERIOD/2) clk <= ~clk; // Forever toggle the clock
    end

    // Set up the inputs to the design. Each line is a clock cycle.

```

initial begin

repeat(1); @(posedge clk);

Reset <= 1; repeat(1) @(posedge clk); // Always reset FSMs at start

Reset <= 0; repeat(100) @(posedge clk);

\$stop; // End the simulation.

end

endmodule

```
module decToHex (score, hex2, hex1, hex0);
```

```
input [8:0] score; //score as input
```

```
output logic [6:0] hex2, hex1, hex0;
```

```
logic [31:0] hund, ten, unit;
```

```
always_comb begin
```

```
hund = score /100; //find hex2 value
```

```
ten = (score /10)%10; //find hex1 value
```

```
unit = score % 10; //find hex0 value
```

```
end
```

```
always_comb begin
```

```
    if (hund == 1) begin
```

```
        hex2 = 7'b1111001;
```

```
    end
```

```
    else if (hund == 2) begin
```

```
        hex2 = 7'b0100100;
```

```
    end
```

```
        else if (hund == 3) begin
```

```
            hex2 = 7'b0110000;
```

```
        end
```

```
            else if (hund == 4) begin
```

```
                hex2 = 7'b0011001;
```

```
end

        else if (hund == 5) begin

            hex2 = 7'b0010010;
        end

        else if (hund == 6) begin

            hex2 = 7'b0000010;
        end

        else if (hund == 7) begin

            hex2 = 7'b1111000;
        end

        else if (hund == 8) begin

            hex2 = 7'b0000000;
        end

        else if (hund == 9) begin

            hex2 = 7'b0010000;
        end

        else if (hund == 0) begin

            hex2 = 7'b1000000;
        end

        else begin

            hex2 = 7'b1;
        end

end
```

```
always_comb begin

    if (ten == 1) begin

        hex1 = 7'b1111001;
    end

    else if (ten == 2) begin
```

```
    hex1 = 7'b0100100;
end

    else if (ten == 3) begin

        hex1 = 7'b0110000;
    end

    else if (ten == 4) begin

        hex1 = 7'b0011001;
    end

    else if (ten == 5) begin

        hex1 = 7'b0010010;
    end

    else if (ten == 6) begin

        hex1 = 7'b0000010;
    end

    else if (ten == 7) begin

        hex1 = 7'b1111000;
    end

    else if (ten == 8) begin

        hex1 = 7'b0000000;
    end

    else if (ten == 9) begin

        hex1 = 7'b0010000;
    end

    else if (ten == 0) begin

        hex1 = 7'b1000000;
    end

    else begin

        hex1 = 7'b1;
    end

end
```

end

always_comb begin

if (unit == 1) begin

 hex0 = 7'b1111001;

end

else if (unit == 2) begin

 hex0 = 7'b0100100;

end

else if (unit == 3) begin

 hex0 = 7'b0110000;

end

else if (unit == 4) begin

 hex0 = 7'b0011001;

end

else if (unit == 5) begin

 hex0 = 7'b0010010;

end

else if (unit == 6) begin

 hex0 = 7'b0000010;

end

else if (unit == 7) begin

 hex0 = 7'b1111000;

end

else if (unit == 8) begin

 hex0 = 7'b0000000;

end

else if (unit == 9) begin

 hex0 = 7'b0010000;


```
        end

        else if (unit == 0) begin

            hex0 = 7'b1000000;

        end

        else begin

            hex0 = 7'b1;

        end

    end

endmodule
```

```
module decToHex_testbench();
```

```
    // Inputs
```

```
    reg [8:0] score;
```

```
    // Outputs
```

```
    wire [6:0] hex2;
```

```
    wire [6:0] hex1;
```

```
    wire [6:0] hex0;
```

```
    decToHex dut (
```

```
        .score(score),
```

```
        .hex2(hex2),
```

```
        .hex1(hex1),
```

```
        .hex0(hex0)
```

```
    );
```

```
    // Display values
```

initial begin

\$monitor("Time=%0d score=%d -> hex2=%b hex1=%b hex0=%b", \$time, score, hex2, hex1, hex0);

end

// Stimulus

initial begin

// Initialize Inputs

score = 0;

// Test cases

#10 score = 9;

#10 score = 10;

#10 score = 21;

#10 score = 32;

#10 score = 43;

#10 score = 54;

#10 score = 65;

#10 score = 76;

#10 score = 87;

#10 score = 98;

#10 score = 99;

#10 score = 100;

#10 score = 111;

#10 score = 123;

#10 score = 134;

#10 score = 145;

#10 score = 156;

#10 score = 167;

```
#10 score = 178;
#10 score = 189;
#10 score = 200;
#10 score = 210;
#10 score = 255;
#10 score = 300;
#10 score = 345;
#10 score = 400;
#10 score = 450;
#10 score = 500;
#10 score = 555;
#10 score = 600;
#10 score = 650;
#10 score = 700;
#10 score = 750;
#10 score = 800;
#10 score = 850;
#10 score = 900;
#10 score = 950;
#10 score = 999;

// End simulation

#10 $finish;

end

endmodule
```

```
module comparator(a, b, out);

input logic [9:0]a;
input logic [9:0]b;
output logic out;

always_comb begin
    out = 0;
    for (int i = 9; i >= 0; i = i - 1) begin
        if (a[i] & ~b[i]) begin
            out = 1;
            break;
        end
        if (~a[i] & b[i]) begin
            out = 0;
            break;
        end
    end
end

endmodule
```

```
module comparator_testbench();
```

```
    logic [9:0]a;
    logic [9:0]b;
    logic out;
```

```
    comparator dut(.a, .b, .out);
```

initial begin

a <= 10'b1111100000; //992

b <= 10'b1100101001; //809

#10;

a <= 10'b1100101001; //809

b <= 10'b1111100000; //992

#10;

a <= 10'b1111100000; //992

b <= 10'b1111100000; //992

#10;

a <= 10'b0; //0

b <= 10'b1; //1

#10;

\$stop; // End the simulation.

end

endmodule

